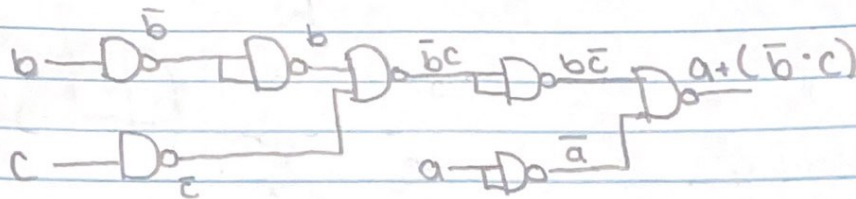


Jalen Powell
Elec 2200


09/01/21

Hw6

1. $a + (\bar{b} \cdot c)$



2.

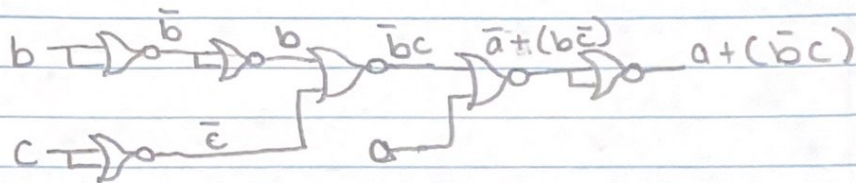

3. A "functionally complete" gate is one which can be used to express all possible truth tables by combining members of the set into a Boolean expression.

