

**Submit a single PDF file online (Canvas) by 10:50 a.m., 3/11 (Thursday).**

**You must show how you get your answer in each problem. The final answer only will receive no credit.**

1. Use the Quine-McCluskey method to find the minimal SOP expression of the function,  $f(A,B,C,D) = \sum m(1, 4, 5, 6, 8, 9, 10, 12, 14)$
2. Use the Quine-McCluskey method to find the minimal SOP expression of the function,  $f(A,B,C,D) = \sum m(0,6,9,10,13) + d(1,3,8)$
3. Design a minimal 2-level NAND realization of the function:  
 $f(A,B,C,D) = \sum m(1,2,3,5,6,7,8,9,12,14)$
4. Repeat Problem 3 for NOR gates.
5. For the (timing) diagram below, find both minimal NAND-NAND and minimal NOR-NOR realizations of the function,  $f(A,B,C)$ .

