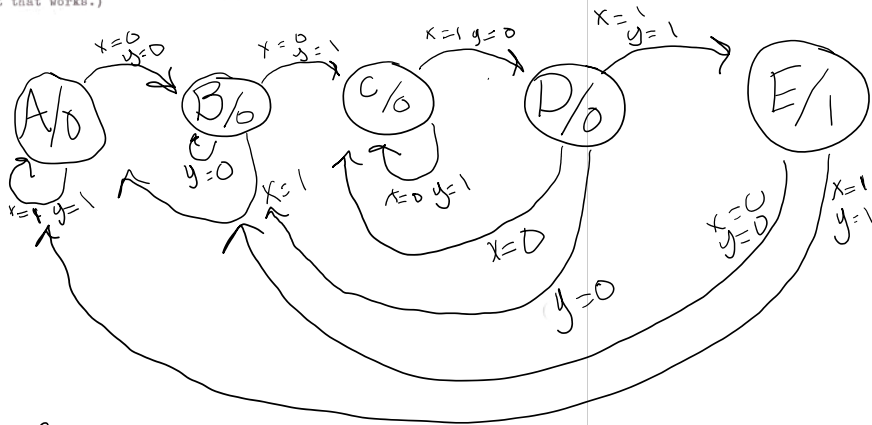


Homework 29

Wednesday, December 1, 2021 1:08 PM

Homework 29 - ELEC 2200 - Fall 2021

Make a one-hot finite state machine using falling edge DFFs (-5 points) to input a 1 only after receiving the sequence 00, 01, 10, 11 on inputs named x and y, respectively. Use only NOR gates. (1 point for gates, 1 point for correct equations for sequence detection/states, 2.5 points for completed circuit that works.)



$$D_A = Q_A xy + Q_B x + Q_E xy$$

$$D_B = Q_A \bar{x} \bar{y} + Q_B \bar{y} + Q_C \bar{y} + Q_E \bar{x} \bar{y}$$

$$D_C = Q_B \bar{x} y + Q_C \bar{x} y + Q_D \bar{x}$$

$$D_D = Q_C x \bar{y}$$

$$D_E = Q_D xy$$

$$Z = Q_E$$

To get to:




A → A, input x=1
input y=1
B, input x=1
E, input x=1
input y=1




B → A, input x=0
input y=0
B, input y=0
D, input y=0
E, input x=0
input y=0

C → B, input x=0
input y=1
C, input x=0
input y=1
D, input x=0

D → C, input x=1
input y=0

E → D, input x=1
input y=1

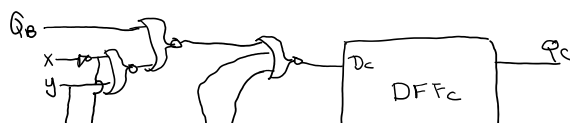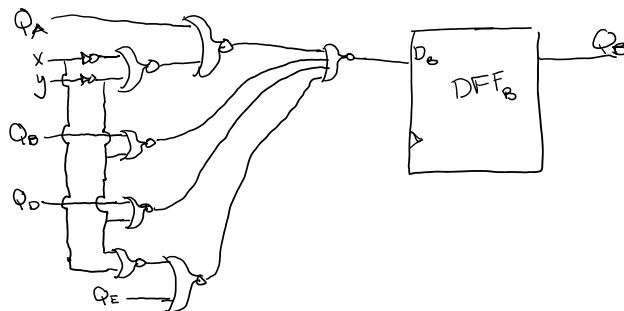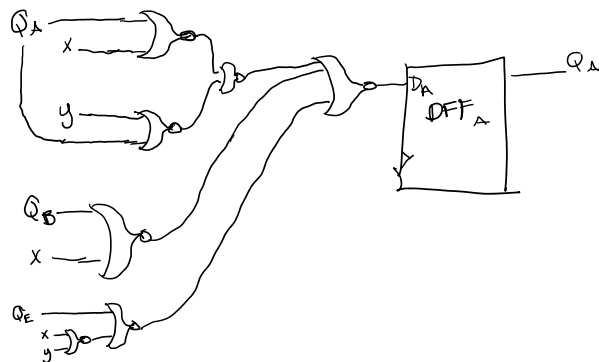

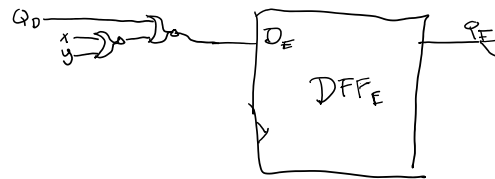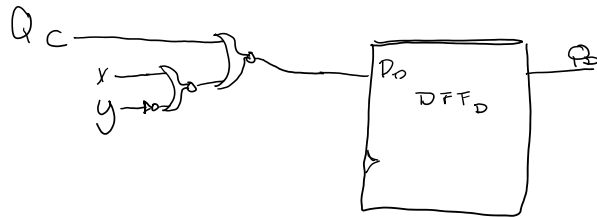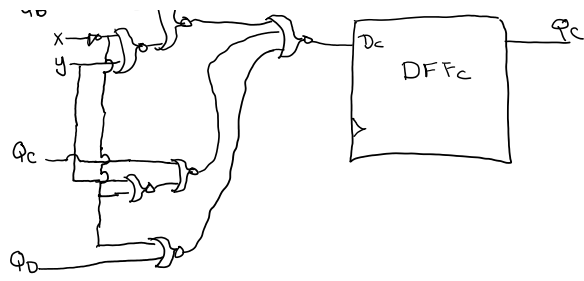

2